

May 30, 2011

- 1) go over answers Ohms Law WS #1-18
- 2) Lab Explanation

reminder of Test Friday

Warm-Up

What is the current flowing through a circuit with a resistance of 12Ω and a voltage of three 1.5V batteries?

$$I = \frac{V}{R} = \frac{4.5V}{12\Omega} = 0.38A$$

Answers Ohms Law Practice Worksheet #1-18

Ohm's Law Lab

Attachments

Answers Series and Parallel Circuit Assignment.notebook

Ohms Law Practice Worksheet Answers.notebook