
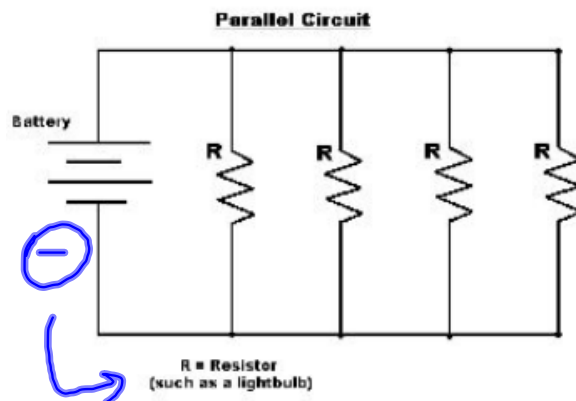
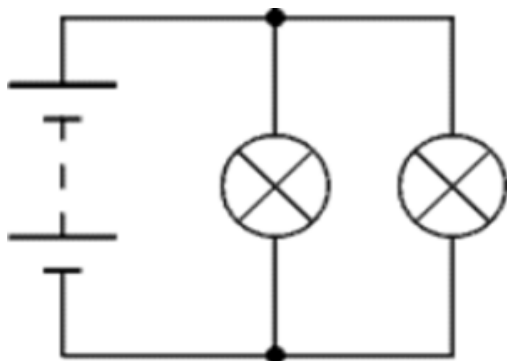
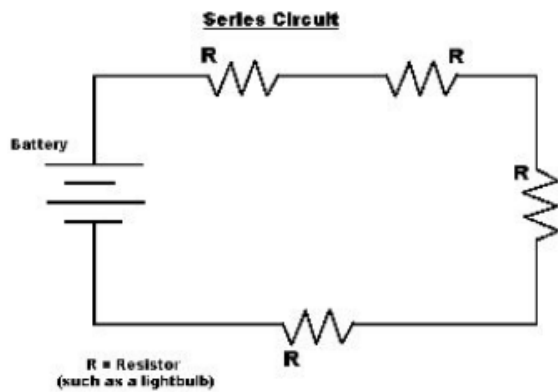


Electric Circuit

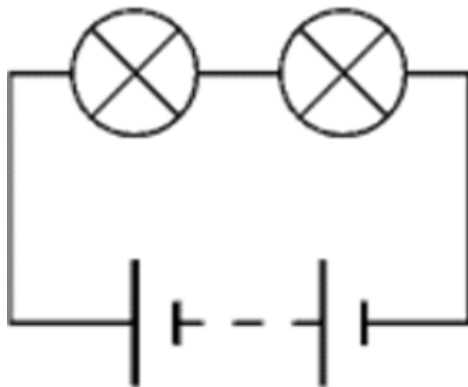- involves the flow of electrons from one place to another
- must contain four aspects: source, control device, conductors, load
- electrons flow from negative terminal of source



Electric Potential

the energy that each electron has as it leaves the source.

Potential Difference (voltage drop) **V**

the energy loss experienced as a current passes through a resistor.

Measured in volts (V).

Current **I**

a measure of the rate at which electric charges move past any given point in the circuit.

Measured in amperes (A).



Resistance **R**

a measure of the ability of a conductor to impede the flow of electrons.

Measured in ohms (Ω)

Quantity	Symbol	Unit of Measurement	Unit Abbreviation
Current	I	Ampere ("Amp")	A
Voltage	V	Volt	V
Resistance	R	Ohm	Ω

Ohm's Law


- Ohm's Law states that the potential difference between two points on a conductor is proportional (directly related) to the electric current flowing through the conductor.
- $V = I \times R$ (voltage drop = electric current x elec. resistance.)

Ohm's Law

Current

$$V = I \times R$$

pot. diff. *resistance*

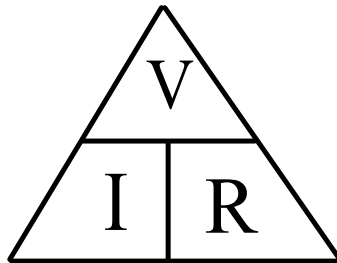


$$\frac{V}{R} = \frac{I \times \cancel{R}}{\cancel{R}}$$

$$I = \frac{V}{R}$$

$$\frac{V}{I} = \frac{\cancel{I} \times R}{\cancel{I}}$$

$$R = \frac{V}{I}$$

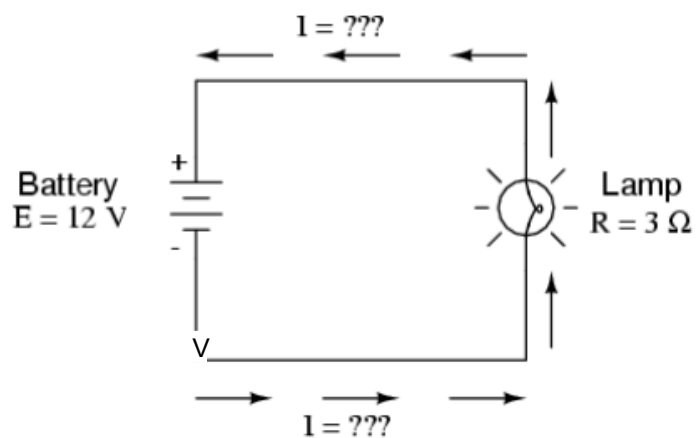

$$V = 12 \text{ V}$$

$$I = ?$$

$$R = 3 \Omega$$

$$V = I \times R$$

$$I = \frac{V}{R} = \frac{12 \text{ V}}{3 \Omega} = \boxed{4 \text{ A}}$$

Sample Problem

Calculate the resistance of an electric circuit that has a voltage of 40.0 V and a current of 7.50 A.

$$V = 40.0 \text{ V}$$

$$I = 7.50 \text{ A}$$

$$R = ?$$

$$V = I \times R$$

$$R = \frac{V}{I}$$

$$R = \frac{40.0 \text{ V}}{7.50 \text{ A}}$$

$$R = 5.33 \Omega$$

Homework

p. 319 #1-3,5,7

Attachments

Answers Series and Parallel Circuit Assignment.notebook