

Science 9 Electricity Exam Review Practice Multiple Choice

- The term "static" means?
  - Always moving
  - Not moving
  - Positive
  - Neutral
- What does the "Law of Electric Charges" state:
  - Like charges repel, and unlike charges attract one another
  - Like charges attract, and unlike charges repel one another
  - Like charges do not respond to each other, and unlike charges attract one another
  - Like charges repel each other, and unlike charges do not respond to each other
- When an object is charged without touching, it is said to be charged by:
  - Friction
  - Contact
  - Induction
  - Static
- The rate at which electric charges flow past a given point in a circuit is called?
  - electric current
  - electrical resistance
  - voltage
  - electric potential
- The type of circuit in which each electrical load is wired to the circuit by its own branch circuit is
  - Series
  - Parallel
  - Secondary
  - primary
- The "electric potential" in a circuit is also known as the:
  - Current
  - Resistance
  - Circuitry
  - Voltage
- What is the charge of an electron?
  - Positive
  - Negative
  - Neutral
  - Stationary
- Which of the following measure the electric current in a circuit?
  - Ammeter
  - Thermometer
  - Voltmeter
  - Ohmmeter
- What is the term for electricity that does not move?
  - Static
  - Current
  - Kinetic
  - Ionic
- A balloon is rubbed on human hair. How will the electrons be transferred?
  - Balloon to hair
  - Hair to balloon
  - Electrons will not move
  - Back and forth between balloon and hair
- Positive charges attract \_\_\_\_ charges.
  - Positive
  - Negative
  - Neutral
  - Both positive and negative
- Electrons can move the easiest through which of the following materials
  - Bread
  - Copper
  - Hair
  - Plastic
- What device measures the electrical energy in a circuit?
  - Ammeter
  - Thermometer
  - Voltmeter
  - Ohmmeter
- In a circuit, what is another name for a light bulb?
  - Source
  - Load
  - Control device
  - Connecting wires

15. A circuit contains three light bulbs in series. Where should a switch be placed to turn all the lights on or off at the same time?
- a. Next to the first light bulb
  - b. Next to the second light bulb
  - c. Next to third bulb
  - d. Anywhere in the circuit
16. Two identical light bulbs are connected in series. How will the brightness of those lights change if another identical bulb is added in series:
- a. Lights will get dimmer
  - b. Lights will get brighter
  - c. Brightness will not change
  - d. One light will brighten the other will dim
17. Using Ohm's law, what is the current drawn from a 12V battery if the circuit contains 5.5 ohms of resistance?
- a. 6.5A
  - b. 0.46A
  - c. 66A
  - d. 2.18A
18. A 2.3A current is drawn from a 24V battery. What is the resistance of the circuit?
- a. 10.4 ohms
  - b. 55.2 ohms
  - c. 0.095 ohms
  - d. 21.7 ohms
19. Using Ohm's law, what is the voltage of a circuit with 2.4ohms of resistance and a current of 4A?
- a. 1.67 volts
  - b. 0.6 volts
  - c. 9.6 volts
  - d. 1.2 volts
20. If one bulb goes out in this type of circuit all the bulbs go out. This circuit is wired in:
- a. Parallel
  - b. Series
  - c. Branches
  - d. Circuit board
21. In a circuit a switch is an example of:
- a. A source
  - b. A load
  - c. Connecting wires
  - d. Control device
22. Two identical light bulbs are connected in parallel. A third identical light is connected in parallel. Theoretically, how will the brightness of the original lights change?
- a. Lights will get dimmer
  - b. Lights will get brighter
  - c. Brightness will not change
  - d. One light will brighten the other will dim
23. Electric potential is measured in:
- a. Amps
  - b. Ohms
  - c. Voltage
  - d. Current
24. Using ohms law, calculate the current in a circuit with 3, 1.5volt batteries and 10 ohms of resistance:
- a. 0.15 A
  - b. 6.67 A
  - c. 0.45A
  - d. 15A
25. A substance that does not allow electrons to pass through it is called a(n):
- a. Conductor
  - b. Capacitor
  - c. Insulator
  - d. Neutral object